

 



 
$$\begin{aligned}
 (a+b) \cdot (a+c) &= a + a \cdot b + a \cdot c + b \cdot c \\
 &= a \cdot (1+b) + a \cdot c + b \cdot c \\
 &= a \cdot (1+c) + b \cdot c \\
 &= a + b \cdot c
 \end{aligned}$$


 
# ECE 410: VLSI Design Course Lecture Notes (Uyemura textbook)






  Professor Andrew Mason  
Michigan State University


 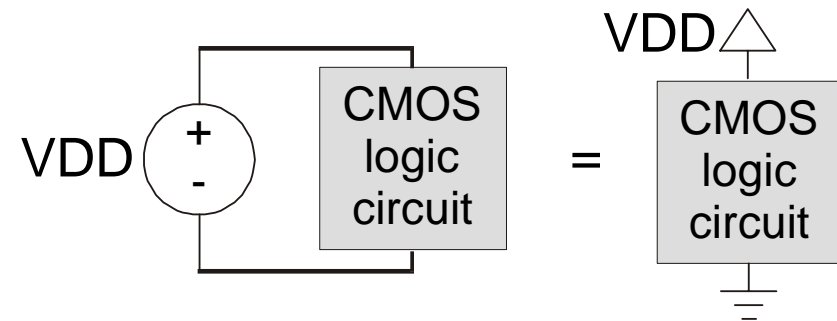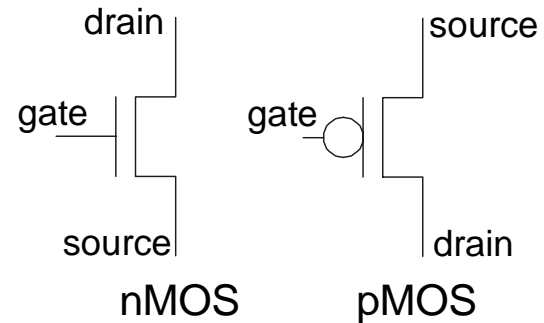
# CMOS Circuit Basics

- **CMOS** = complementary MOS
  - uses 2 types of MOSFETs to create logic functions
    - nMOS
    - pMOS
- CMOS Power Supply
  - typically single power supply
  - **VDD**, with Ground reference
    - typically uses single power supply
    - VDD varies from 5V to 1V
- Logic Levels
  - all voltages between 0V and VDD
  - Logic '1' = VDD
  - Logic '0' = ground = 0V




# Transistor Switching Characteristics

- nMOS

- switching behavior

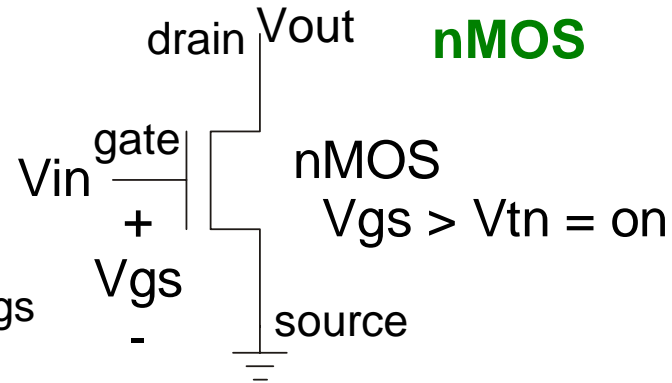
- on = closed, when  $V_{in} > V_{tn}$ 
  - $V_{tn}$  = nMOS “threshold voltage”
  - $V_{in}$  is referenced to ground,  $V_{in} = V_{gs}$
- off = open, when  $V_{in} < V_{tn}$



- pMOS

- switching behavior

- on = closed, when  $V_{in} < VDD - |V_{tp}|$ 
  - $|V_{tp}|$  = pMOS “threshold voltage” magnitude
  - $V_{in}$  is referenced to ground,  $V_{in} = VDD - V_{sg}$
- off = open, when  $V_{in} > VDD - |V_{tp}|$

 

Rule to Remember: 'source' is at


- lowest potential for nMOS
- highest potential for pMOS



# Transistor Digital Behavior



- nMOS

$V_{in}$	$V_{out}$ (drain)
1	$V_s=0$ device is ON
0	? device is OFF

 

- pMOS

$V_{in}$	$V_{out}$ (drain)
1	? device is OFF
0	$V_s=V_{DD}=1$ device is ON

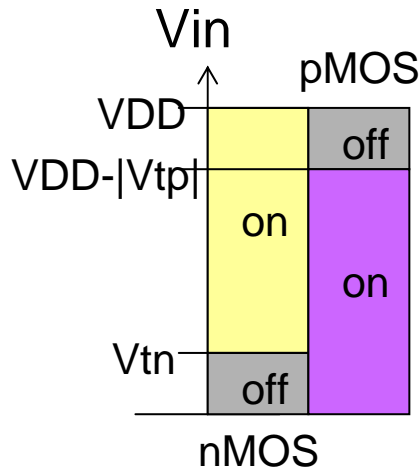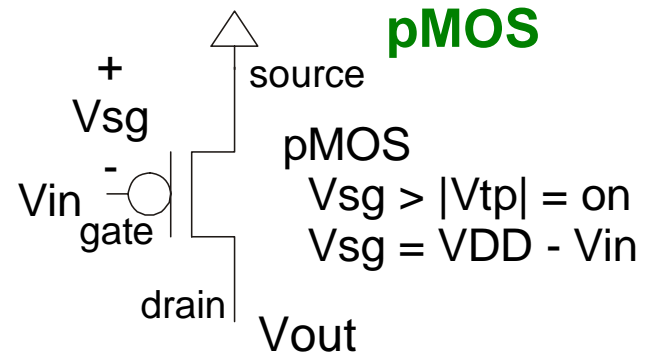



Notice:

When  $V_{in}$  = low, nMOS is off, pMOS is on  
 When  $V_{in}$  = high, nMOS is on, pMOS is off  
 → Only one transistor is on for each digital voltage


  
# MOSFET Pass Characteristics

- Pass characteristics: passing of voltage from drain (or source) to source (or drain) when device is ON (via gate voltage)
- Each type of transistor is better than the other at passing (to output) one digital voltage
  - nMOS passes a good low (0) but not a good high (1)
  - pMOS passes a good high (1) but not a good low (0)



## Rule to Remember

'source' is at lowest potential for nMOS and at highest potential for pMOS



# MOSFET Terminal Voltages

- How do you find one terminal voltage if the other 2 are known?

- nMOS


- case 1) if  $V_g > V_i + V_{tn}$ , then  $V_o = V_i$  ( $V_g - V_i > V_{tn}$ )

- here  $V_i$  is the "source" so the nMOS will pass  $V_i$  to  $V_o$

- case 2) if  $V_g < V_i + V_{tn}$ , then  $V_o = V_g - V_{tn}$  ( $V_g - V_i < V_{tn}$ )

- here  $V_o$  is the "source" so the nMOS output is limited

For nMOS,  $\max(V_o) = V_g - V_{tn}$

 

- pMOS

- case 1) if  $V_g < V_i - |V_{tp}|$ , then  $V_o = V_i$  ( $V_i - V_g > |V_{tp}|$ )

- here  $V_i$  is the "source" so the pMOS will pass  $V_i$  to  $V_o$

- case 2) if  $V_g > V_i - |V_{tp}|$ , then  $V_o = V_g + |V_{tp}|$  ( $V_i - V_g < |V_{tp}|$ )

- here  $V_o$  is the "source" so the pMOS output is limited

For pMOS,  $\min(V_o) = V_g + |V_{tp}|$

## IMPORTANT:

Rules only apply if the devices is ON (e.g.,  $V_g > V_{tn}$  for nMOS)




# MOSFET Terminal Voltages: Examples

- nMOS rules  $\max(V_o) = V_g - V_{tn}$

- case 1) if  $V_g > V_i + V_{tn}$ , then  $V_o = V_i$  ( $V_g - V_i > V_{tn}$ )
- case 2) if  $V_g < V_i + V_{tn}$ , then  $V_o = V_g - V_{tn}$  ( $V_g - V_i < V_{tn}$ )

• nMOS examples ( $V_{tn}=0.5V$ )

 - 1:  $V_g=5V$ ,  $V_i=2V$ 
  - $V_g=5 > V_i + V_{tn} = 2.5 \Rightarrow V_o = 2V$
- 2:  $V_g=2V$ ,  $V_i=2V$ 
  - $V_g=2 < V_i + V_{tn} = 2.5 \Rightarrow V_o = 1.5V$




- pMOS rules  $\min(V_o) = V_g + |V_{tp}|$

- case 1) if  $V_g < V_i - |V_{tp}|$ , then  $V_o = V_i$  ( $V_i - V_g > |V_{tp}|$ )
- case 2) if  $V_g > V_i - |V_{tp}|$ , then  $V_o = V_g + |V_{tp}|$  ( $V_i - V_g < |V_{tp}|$ )

• pMOS examples ( $V_{tp}=-0.5V$ )

- 1:  $V_g=2V$ ,  $V_i=5V$ 
  - $V_g=2 < V_i - |V_{tp}| = 4.5 \Rightarrow V_o = 5V$
- 2:  $V_g=2V$ ,  $V_i=2V$ 
  - $V_g=2 > V_i - |V_{tp}| = 1.5 \Rightarrow V_o = 2.5V$

 

# Switch-Level Boolean Logic

- Logic gate are created by using sets of controlled switches
- Characteristics of an **assert-high** switch




**nMOS** acts like an **assert-high** switch

**Figure 2.1** Behavior of an assert-high switch

–  $y = x \cdot A$ , i.e.  $y = x$  if  $A = 1$   
 AND, or multiply function


Series switches  $\Rightarrow$  AND function

 

**Figure 2.2** Series-connected switches

$a$  AND  $b$

Parallel switches  $\Rightarrow$  OR function

 

**Figure 2.4** Parallel-connected switches


$a$  OR  $b$





 
# Switch-Level Boolean Logic

- Characteristics of an **assert-low** switch



(a) Closed

 


(b) Open

**pMOS** acts like an **assert-low** switch


–  $y = x \cdot \bar{A}$ , i.e.  $y = x$  if  $A = 0$

error in figure 2.5

 Series assert-low switches  $\Rightarrow ?$



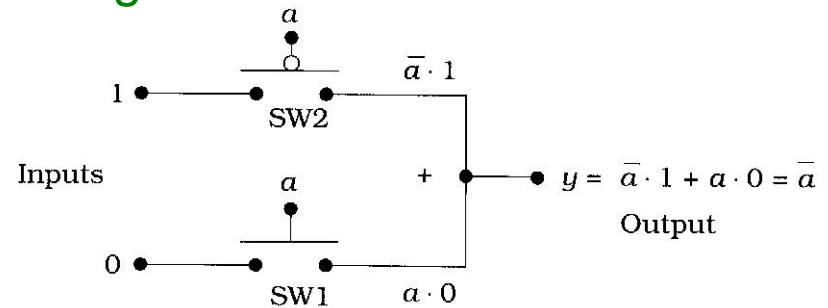**NOT function**, combining assert-high and assert-low switches



Remember This??

$$\bar{a} \cdot \bar{b} = \overline{a + b}, \quad \bar{a} + \bar{b} = \overline{a \cdot b}$$

DeMorgan relations

$a=1 \Rightarrow$  SW1 closed, SW2 open  $\Rightarrow y=0 = \bar{a}$

$a=0 \Rightarrow$  SW1 open, SW2 closed  $\Rightarrow y=1 = \bar{a}$



# CMOS "Push-Pull" Logic


- CMOS Push-Pull Networks

- pMOS

- "on" when input is low
- pushes output high

- nMOS

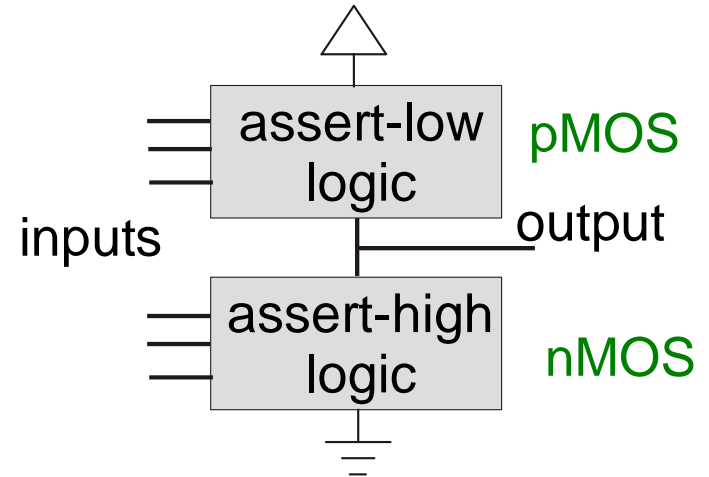- "on" when input is high
- pulls output low




- Operation: for a given logic function

- one logic network (p or n) produces the logic function and pushes or pulls the output
- the other network acts as a "load" to complete the circuit, but is turned off by the logic inputs
- since only one network is active, there is no static current (between VDD and ground)
  - zero static power dissipation


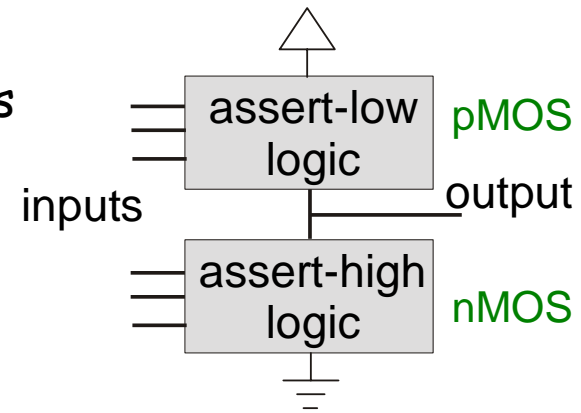
# Creating Logic Gates in CMOS

- All standard Boolean logic functions (INV, NAND, OR, etc.) can be produced in CMOS push-pull circuits.
- Rules for constructing logic gates using CMOS
  - use a complementary nMOS/pMOS pair for each input
  - connect the output to VDD through pMOS txs
  - connect the output to ground through nMOS txs
  - insure the output is always either high or low
- CMOS produces "inverting" logic
  - CMOS gates are based on the inverter
  - outputs are always inverted logic functions  
e.g., NOR, NAND rather than OR, AND



## Logic Properties

### DeMorgan's Rules

$$(a \cdot b)' = a' + b'$$

$$(a + b)' = a' \cdot b'$$

### Useful Logic Properties

$$1 + x = 1 \quad 0 + x = x$$

$$1 \cdot x = x \quad 0 \cdot x = 0$$

$$x + x' = 1 \quad x \cdot x' = 0$$

$$a \cdot a = a \quad a + a = a$$

$$ab + ac = a(b+c)$$

### Properties which can be proven


$$(a+b)(a+c) = a+bc$$

$$a + a'b = a + b$$




# Review: Basic Transistor Operation

## CMOS Circuit Basics

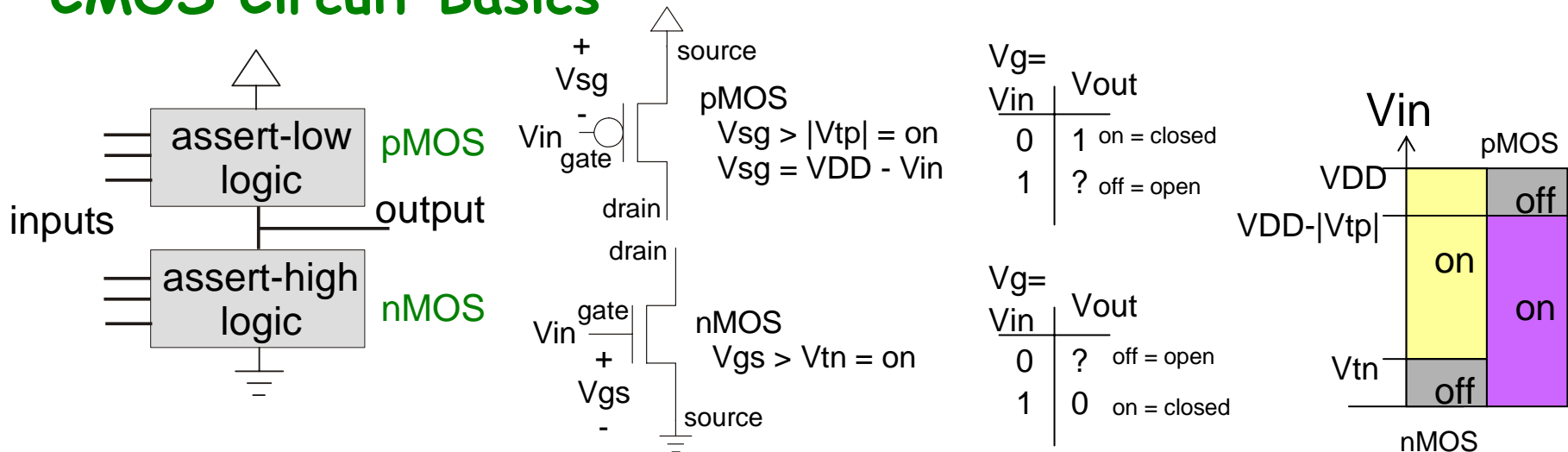
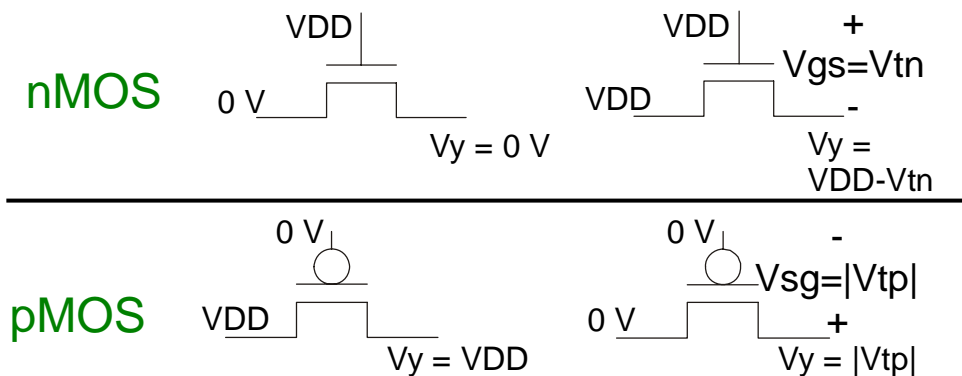
## CMOS Pass Characteristics

'source' is at lowest potential (nMOS) and highest potential (pMOS)




- nMOS
  - 0 in  $\rightarrow$  0 out
  - VDD in  $\rightarrow$   $V_{DD} - V_{tn}$  out
  - strong '0', weak '1'
- pMOS
  - VDD in  $\rightarrow$  VDD out
  - 0 in  $\rightarrow$   $|V_{tp}|$  out
  - strong '1', weak '0'



 
# Review: Switch-Level Boolean Logic

- **assert-high switch**

- $y = x \cdot A$ , i.e.  $y = x$  if  $A = 1$




(a) Open

 

(b) Closed


- series = AND

 

assert-high switch

**a AND b**


- parallel = OR

 

 
**a OR b**

- **assert-low switch**

- $y = x \cdot \bar{A}$ , i.e.  $y = x$  if  $A = 0$




(a) Closed

 

(b) Open

- series = NOR

- parallel = NAND

 


**NOT (a OR b)**



# CMOS Inverter

- Inverter Function
  - toggle binary logic of a signal



- Inverter Symbol

 

- Inverter Switch Operation

- Inverter Truth Table

$x$	$y = \overline{x}$
0	1
1	0

  


input low  $\rightarrow$  output high  
 nMOS off/open  
 pMOS on/closed

input high  $\rightarrow$  output low  
 nMOS on/closed  
 pMOS off/open

pMOS “on”  
 $\rightarrow$  output high (1)

nMOS “on”  
 $\rightarrow$  output low (0)


- CMOS Inverter Schematic

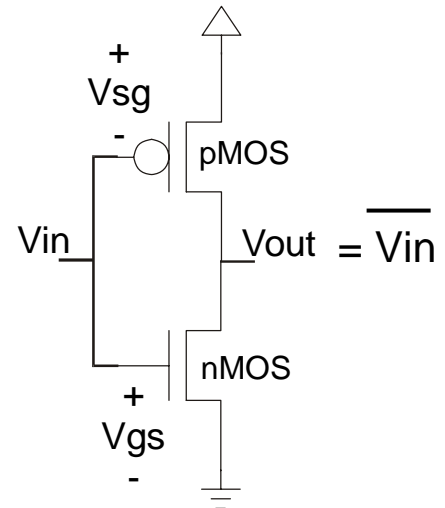

# nMOS Logic Gates

- We will look at nMOS logic first, more simple than CMOS
- nMOS Logic (no pMOS transistors)
  - assume a resistive load to VDD
  - nMOS switches pull output low based on inputs



## nMOS Inverter

 

(a) nMOS is **off**  
 → output is high (1)



(b) nMOS is **on**  
 → output is low (0)

## nMOS NOR

  

- parallel switches = OR function
- nMOS pulls low (NOTs the output)

## nMOS NAND

  


- series switches = AND function
- nMOS pulls low (NOTs the output)



# CMOS NOR Gate


- NOR Symbol

 

- NOR Truth Table

x	y	$\overline{x+y}$
0	0	1
0	1	0
1	0	0
1	1	0

- Karnaugh map

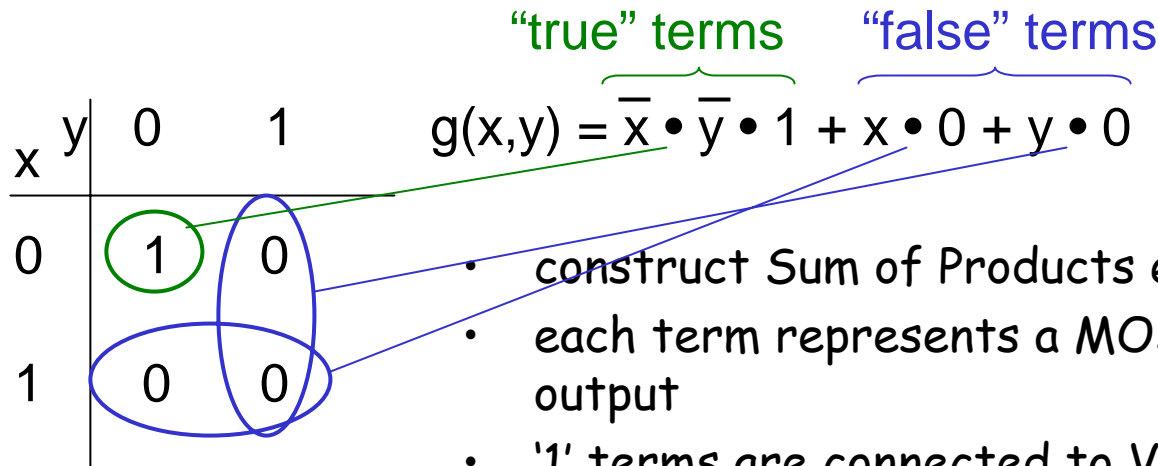


- construct Sum of Products equation with all terms
- each term represents a MOSFET path to the output
- '1' terms are connected to VDD via pMOS
- '0' terms are connected to ground via nMOS





# CMOS NOR Gate

- CMOS NOR Schematic

 

$$g(x,y) = \overline{x} \cdot \overline{y} \cdot 1 + x \cdot 0 + y \cdot 0$$

- output is LOW if x OR y is true
  - parallel nMOS
- output is HIGH when x AND y are false
  - series pMOS


- Notice: series-parallel arrangement

- when nMOS in series, pMOS in parallel, and visa versa
- true for all *static CMOS* logic gates
- allows us to construct more complex logic functions



# CMOS NAND Gate


- NAND Symbol

 


- Truth Table

x	y	$\overline{x \cdot y}$
0	0	1
0	1	1
1	0	1
1	1	0

- K-map

 

- CMOS Schematic

 



$$g(x,y) = (\bar{y} \cdot 1) + (\bar{x} \cdot 1) + (x \cdot y \cdot 0)$$

- output is LOW if x AND y are true
  - series nMOS
- output is HIGH when x OR y is false
  - parallel pMOS




# 3-Input Gates

- NOR3

  


$$g(x,y) = \overline{x+y+z}$$

- NAND3

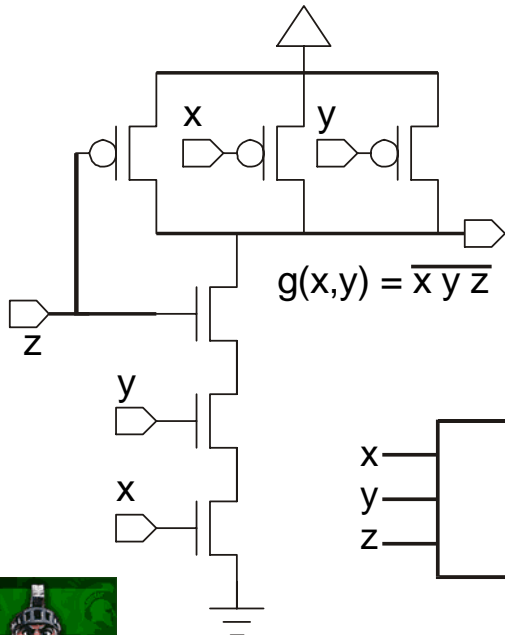


$$g(x,y) = \overline{x y z}$$

 

- Alternate Schematic

- what function?

 

- note shared gate inputs
  - is input order important?
  - in series, parallel, both?
- this schematic resembles how the circuit will look in *physical layout*



# Complex Combinational Logic

---

- General logic functions
  - for example

$$f = \overline{a \cdot (b + c)}, \quad f = \overline{(d \cdot e) + a \cdot (\overline{b} + c)}$$

- How do we construct the CMOS gate?
  - use DeMorgan principles to modify expression
    - construct nMOS and pMOS networks

$$\overline{a \cdot b} = \overline{a} + \overline{b}$$

$$\overline{a + b} = \overline{a} \cdot \overline{b}$$

- use Structured Logic (covered only briefly in ECE410)
  - AOI (AND OR INV)
  - OAI (OR AND INV)




# Using DeMorgan

- DeMorgan Relations


- NAND-OR rule  $a \cdot b = \overline{\overline{a} + \overline{b}}$

- bubble pushing illustration

 


- bubbles = inversions

 - NOR-AND rule  $a + b = \overline{\overline{a} \cdot \overline{b}}$




to implement pMOS this way, must push all bubbles to the inputs and remove all NAND/NOR output bubbles

 - pMOS and bubble pushing
  - Parallel-connected pMOS



- assert-low OR
- creates NAND function

- Series-connected pMOS

 


- assert-low AND
- creates NOR function




# Review: CMOS NAND/NOR Gates

- NOR Schematic

 

- output is LOW if x OR y is true
  - parallel nMOS
- output is HIGH when x AND y are false
  - series pMOS

- NAND Schematic

 

- output is LOW if x AND y are true
  - series nMOS
- output is HIGH when x OR y is false
  - parallel pMOS



# Rules for Constructing CMOS Gates

## The Mathematical Method

- Given a logic function

$$F = f(a, b, c)$$

- Reduce (using DeMorgan) to eliminate inverted operations
  - inverted variables are OK, but not operations (NAND, NOR)


- Form pMOS network by complementing the **inputs**

$$F_p = f(\bar{a}, \bar{b}, \bar{c})$$

- Form the nMOS network by complementing the **output**

$$F_n = \overline{f(a, b, c)} = \bar{F}$$

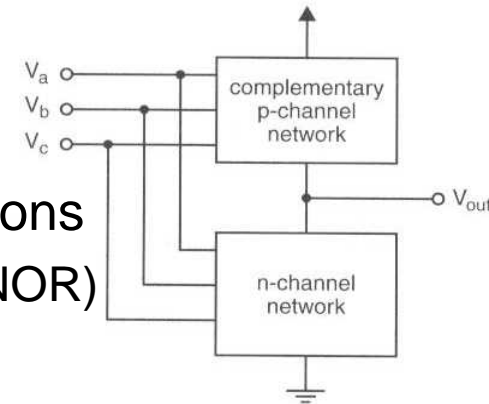- Construct  $F_n$  and  $F_p$  using AND/OR series/parallel MOSFET structures
  - series = AND, parallel = OR




## EXAMPLE:

$$F = \overline{ab} \Rightarrow$$

$$F_p = \overline{\overline{a} \overline{b}} = a+b; \quad \text{OR/parallel}$$

 
$$F_n = \overline{\overline{ab}} = ab; \quad \text{AND/series}$$



# CMOS Combinational Logic Example

- Construct a CMOS logic gate to implement the function:

$$F = \overline{a \cdot (b + c)}$$

 

14 transistors (cascaded gates)

## pMOS

- Apply DeMorgan expansions


$$F = \overline{a + (b + c)}$$

$$F = \overline{a} + (\overline{b} \cdot \overline{c})$$

- Invert inputs for pMOS

$$F_p = a + (b \cdot c)$$

- Resulting Schematic

 


## nMOS

- Invert output for nMOS


$$F_n = a \cdot (b + c)$$

- Apply DeMorgan none needed

- Resulting Schematic

 

6 transistors (CMOS)

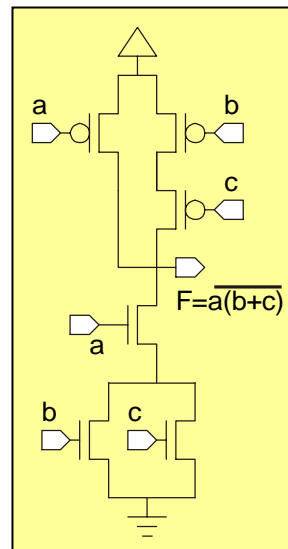



# Structured Logic

---


- Recall CMOS is inherently Inverting logic
- Can use structured circuits to implement general logic functions
- **AOI**: implements logic function in the order AND, OR, NOT (Invert)
  - Example:  $F = a \cdot b + c \cdot d$ 
    - operation order: i) a AND b, c AND d, ii) (ab) OR (cd), iii) NOT
  - Inverted Sum-of-Products (SOP) form
- **OAI**: implements logic function in the order OR, AND, NOT (Invert)
  - Example:  $G = (x+y) \cdot (z+w)$ 
    - operation order: i) x OR y, z OR w, ii) (x+y) AND (z+w), iii) NOT
  - Inverted Product-of-Sums (POS) form
- Use a *structured CMOS array* to realize such functions




# AOI/OAI nMOS Circuits

- nMOS AOI structure

- series txs in parallel

 


$$X = \overline{a \cdot b + c \cdot d}$$

 


- nMOS OAI structure

- series of parallel txs

 

$$Y = \overline{a + e \cdot b + f}$$

 


error in textbook Figure 2.45


 
# AOI/OAI pMOS Circuits


- pMOS AOI structure

- series of parallel txs
- opposite of nMOS (series/parallel)




- pMOS OAI structure

 
- series txs in parallel
- opposite of nMOS (series/parallel)



Complete CMOS  
AOI/OAI circuits

 

(a) AOI circuit

 

(b) OAI circuit



# Implementing Logic in CMOS

---

- Reducing Logic Functions
  - fewest operations  $\Rightarrow$  fewest txs
  - minimized function to eliminate txs
  - Example:  $x y + x z + x v = x (y + z + v)$ 

5 operations:	3 operations:
3 AND, 2 OR	1 AND, 2 OR
# txs = ___?	# txs = ___?
- Suggested approach to implement a CMOS logic function
  - create nMOS network
    - invert output
    - reduce function, use DeMorgan to eliminate NANDs/NORs
    - implement using **series for AND** and **parallel for OR**
  - create pMOS network
    - complement each operation in nMOS network
      - i.e. make parallel into series and visa versa



# CMOS Logic Example

- Construct the function below in CMOS

$$F = a + b \cdot (c + d); \text{ remember AND operations occur before OR}$$

- nMOS


- Group 1: c & d in parallel
- Group 2: b in series with G1
- Group 3: a parallel to G2

follow same order in pMOS

don't compliment inputs

- pMOS

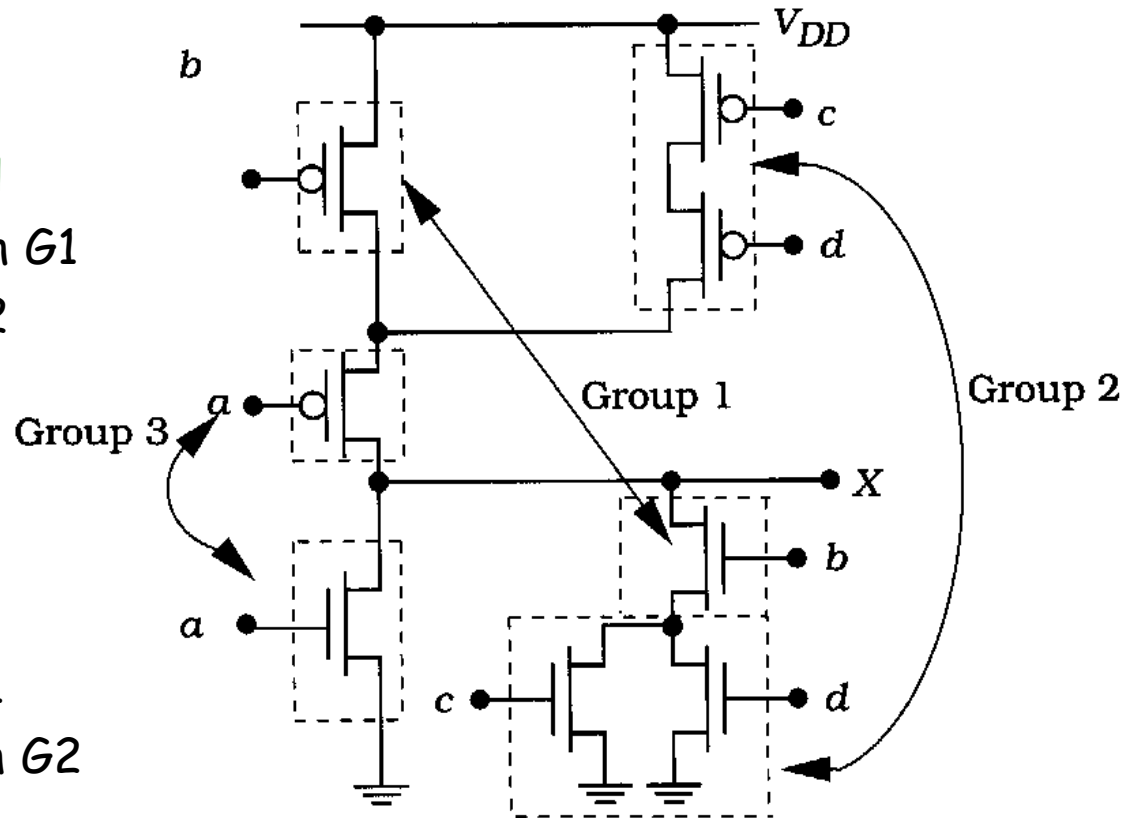- Group 1: c & d in series
- Group 2: b parallel to G1
- Group 3: a in series with G2



- Circuit has an OAOI organization (AOI with extra OR)



# Another Combinational Logic Example

---

- Construct a CMOS logic gate which implements the function:

$$F = \overline{a} \cdot (b + \overline{c})$$

- pMOS

- Apply DeMorgan expansions  
none needed
- Invert inputs for pMOS  
 $F_p = a \cdot (\overline{b} + c)$
- Resulting Schematic ?

- nMOS

- Invert output for nMOS  
 $F_n = \overline{a} \cdot (b + \overline{c})$
- Apply DeMorgan  
 $F_n = a + (\overline{b+c})$   
 $F_n = a + (\overline{b} \cdot c)$
- Resulting Schematic ?



# Yet Another Combinational Logic Example

- Implement the function below by constructing the nMOS network and complementing operations for the pMOS:

$$F = \overline{\overline{a}} \cdot b \cdot (a + c)$$

- nMOS

- Invert Output

- $F_n = \overline{\overline{a}} \cdot b \cdot (a + c) = \overline{a} \cdot b + \overline{(a + c)}$

- Eliminate NANDs and NORs

- $F_n = \overline{a} \cdot b + (\overline{a} \cdot \overline{c})$


- Reduce Function

- $F_n = \overline{a} \cdot (b + \overline{c})$

- Resulting Schematic ?

- Complement operations for pMOS

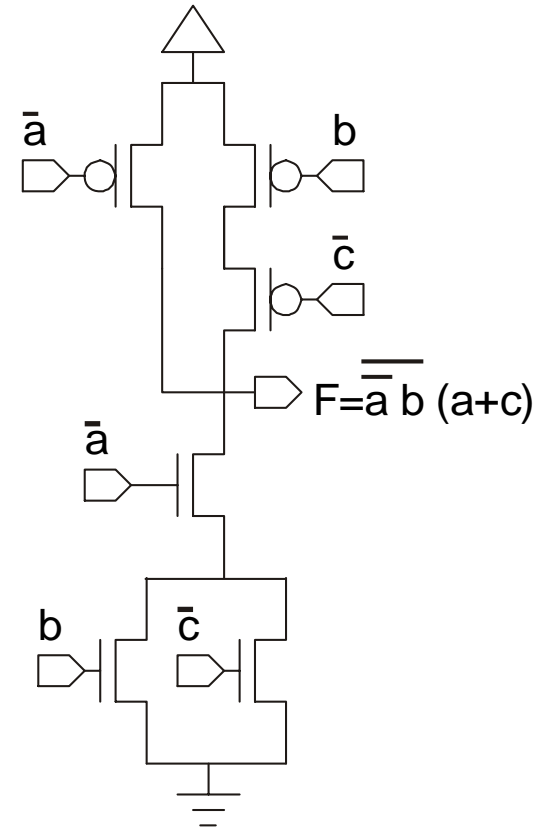- $F_p = \overline{a} + (b \cdot \overline{c})$




# XOR and XNOR

- Exclusive-OR (XOR)

- $a \oplus b = \bar{a} \cdot b + a \cdot \bar{b}$

- not AOI form (no "I")

 

a	b	a ⊕ b
0	0	0
0	1	1
1	0	1
1	1	0

- Exclusive-NOR

- $\overline{a \oplus b} = a \cdot b + \bar{a} \cdot \bar{b}$

- inverse of XOR

- XOR/XNOR in AOI form

- XOR:  $\overline{\overline{a \oplus b}} = \overline{a \cdot b + \bar{a} \cdot \bar{b}}$ , formed by complementing XNOR above


- XNOR:  $\overline{a \oplus b} = \overline{\overline{a \cdot b + \bar{a} \cdot \bar{b}}}$ , formed by complementing XOR

thus, interchanging a and  $\bar{a}$  (or b and  $\bar{b}$ ) converts from XOR to XNOR






# XOR and XNOR AOI Schematic

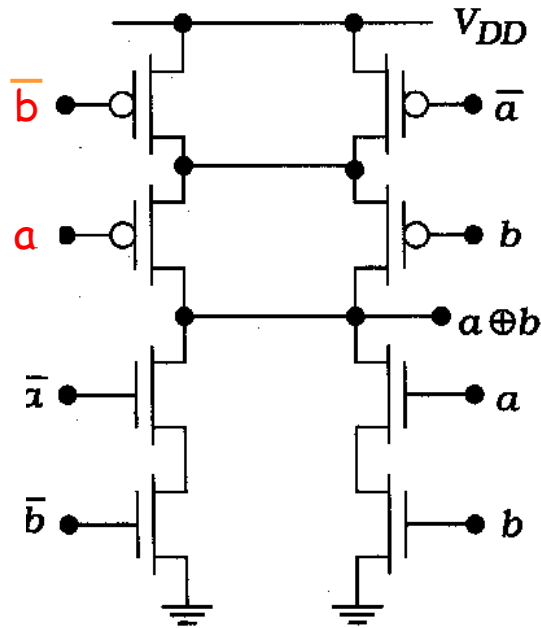

(a) Exclusive-OR

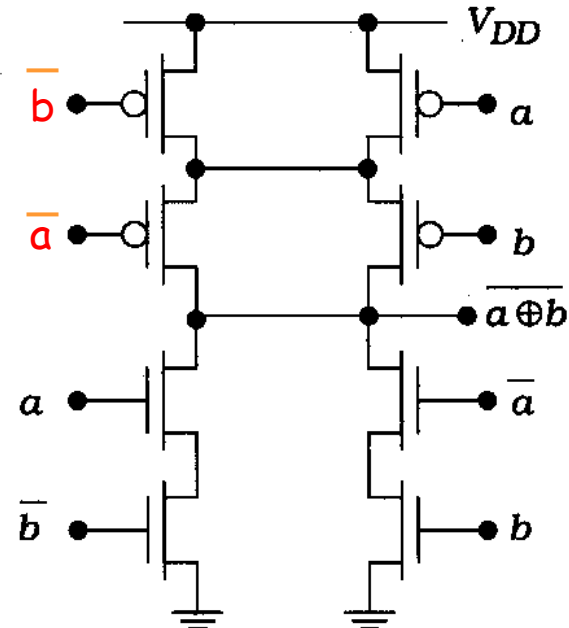

(b) Exclusive-NOR

note: errors in textbook figure

$$\text{-XOR: } a \oplus b = \overline{a \cdot b + \bar{a} \cdot \bar{b}}$$

$$\text{-XNOR: } \overline{a \oplus b} = \overline{\overline{a \cdot b + a \cdot \bar{b}}}$$

uses exact same structure as generic AOI





# CMOS Transmission Gates

- Function

recall: pMOS passes a good '1'  
and nMOS passes a good '0'

- gated switch, capable of passing both '1' and '0'

- Formed by a parallel nMOS and pMOS tx

  

- Controlled by gate select signals,  $s$  and  $\bar{s}$

- if  $s = 1$ ,  $y = x$ , switch is closed, txs are on

- if  $s = 0$ ,  $y = \text{unknown}$  (high impedance),  
switch open, txs off


$$y = x s, \text{ for } s=1$$



# Transmission Gate Logic Functions

- TG circuits used extensively in CMOS
  - good switch, can pass full range of voltage (VDD-ground)
- 2-to-1 MUX using TGs

$$F = P_0 \cdot \bar{s} + P_1 \cdot s$$

 


$s$	TG0	TG1	$F$
0	Closed	Open	$P_0$
1	Open	Closed	$P_1$

 
# More TG Functions

- TG XOR and XNOR Gates

$$\overline{a \oplus b} = a \cdot b + \bar{a} \cdot \bar{b}$$



(a) XOR circuit

 

(b) XNOR circuit

- Using TGs instead of "static CMOS"
  - TG OR gate

